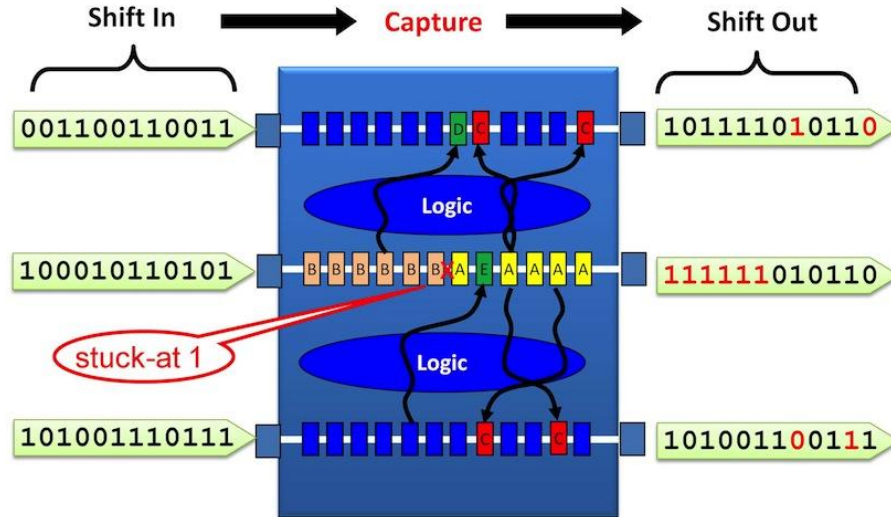


CPE 470 - Design For Test




DFT

- Bringing Up Chips after Fabrication is hard
 - Billions of transistors each will failure risk
- Can be really hard to diagnose issues without view into the system
- **DFT**: methodology or design principles to ensure design is testable at the post fabrication stage
 - Same acronym, but not a Discrete Fourier Transform
- Build system with ways of debugging its internal pieces
 - Trade off logic area for higher ability to diagnose issues
- Build configuration features in
 - Ability to disable or power off certain parts of chip if they don't work

Scan Chain Topology

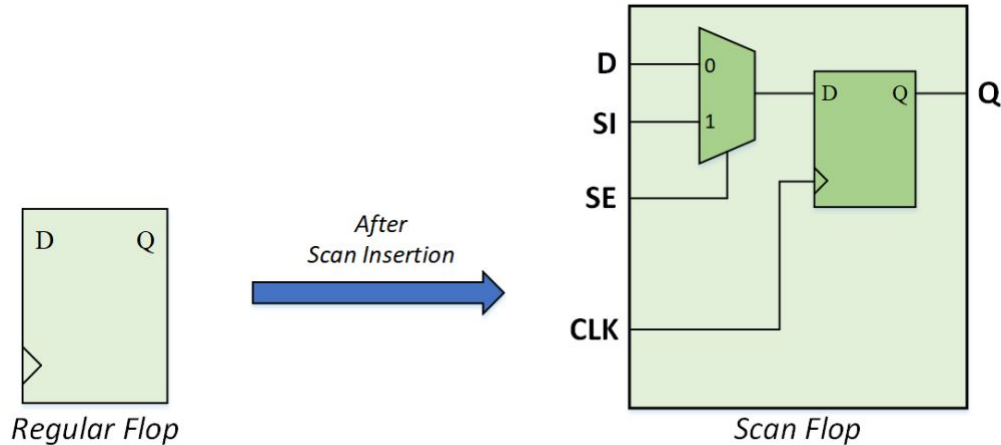
- Problem: How can we most easily debug every element in our design?
- Solution: Conditionally connect EVERY flip flop in a serial shift register
 - How do we do this?
- Replace every Register with a Scan Chain Register
 - Register + Mux that selects between normal operation and scan mode
 - When Scan Enable is active, every flip flop in design becomes a shift register



- Use Scan Chain to read or write values to each flip flop

Scan Chain Topology


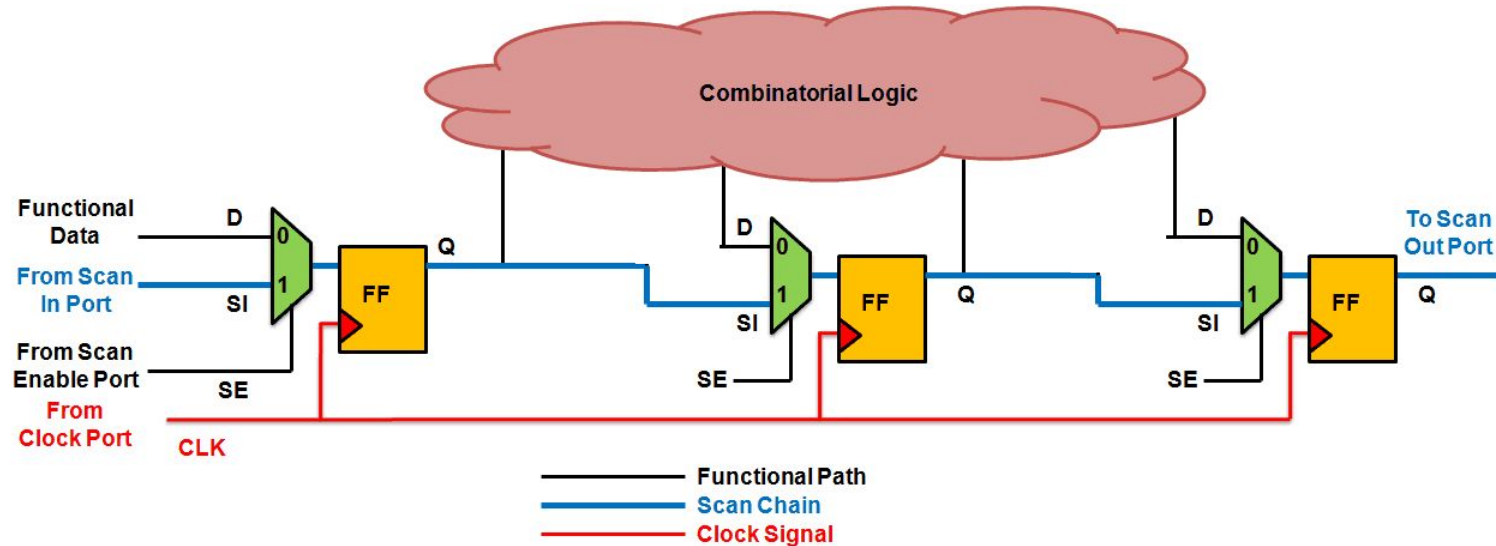
- All Flip-Flop Outputs feed into combinational logic AND next Flip Flop in chain
- Combinational logic could be many gates!
 - Can't expose the output of every logic gate, only ends of combination paths
- Data shifted in on Scan In and out on Scan Out
 - Usually Scan Chain also has some way to single-step the clock



Scan Chain Example

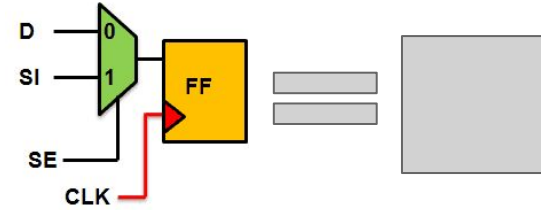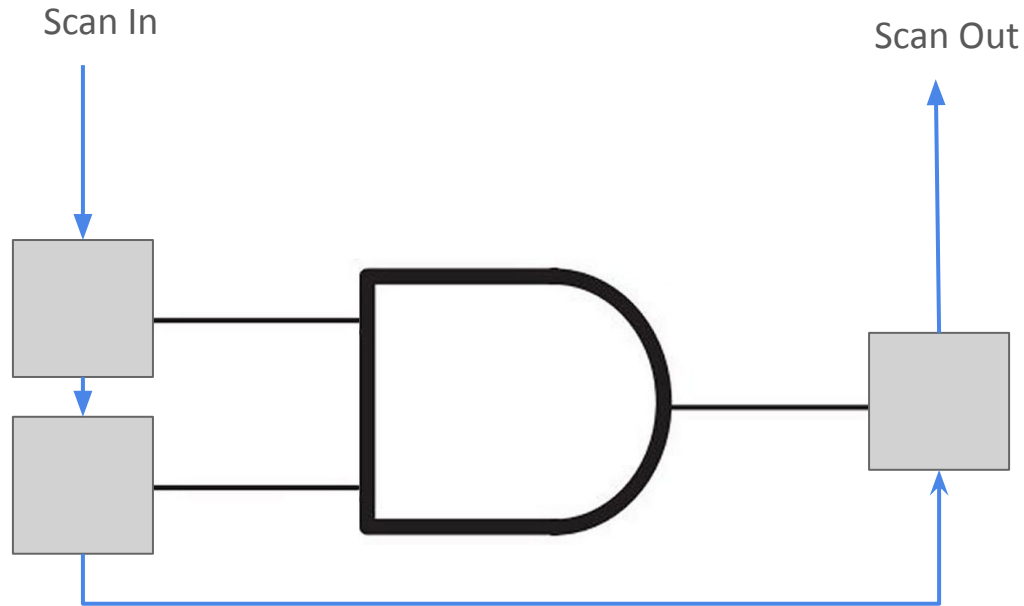Example: Test that all flip flops work



- Set Scan Enable
- **Shift in 000**
- Shift Out and check equal
- **Shift in 111**
- Shift Out and check equal
- Lower Scan Enable



Scan Chain Example

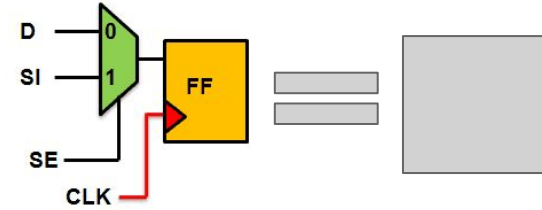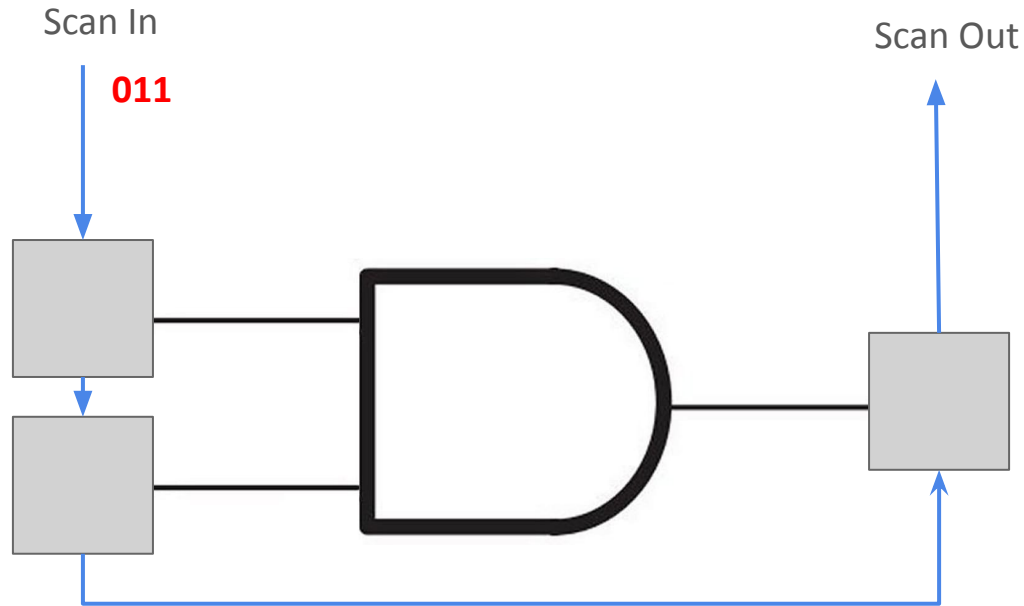Example: Test And Gate



- Enable Scan
- **Shift in 011 (MSB)**
- Disable Scan
- Step the clock
- Enable Scan
- Check for **1** on scan out



Scan Chain Example

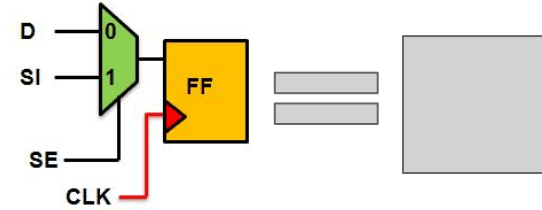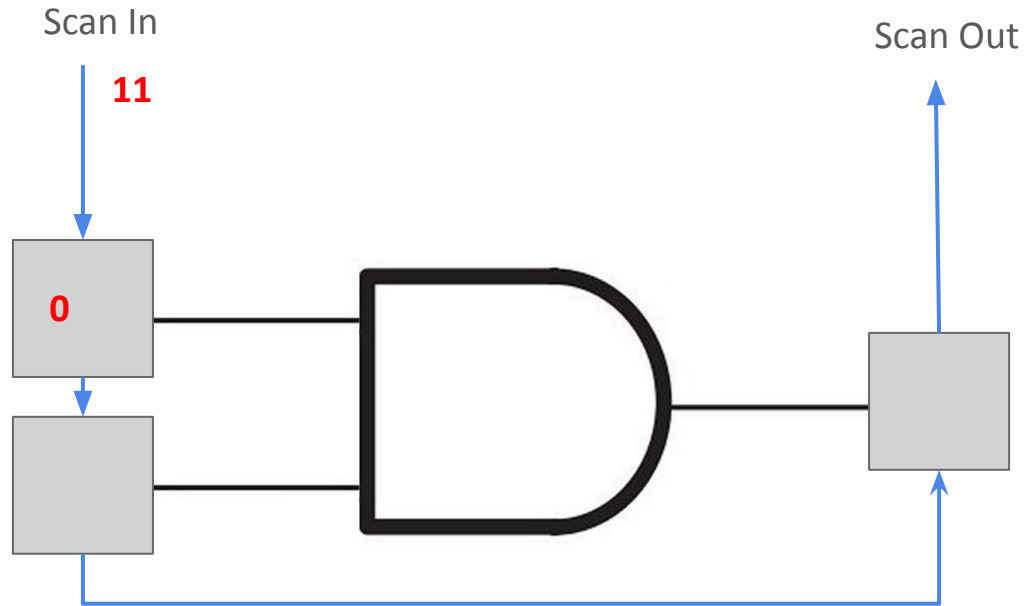Example: Test And Gate



- Enable Scan
- **Shift in 011 (MSB)**
- Disable Scan
- Step the clock
- Enable Scan
- Check for **1** on scan out



Scan Chain Example

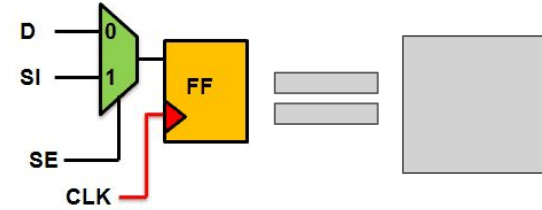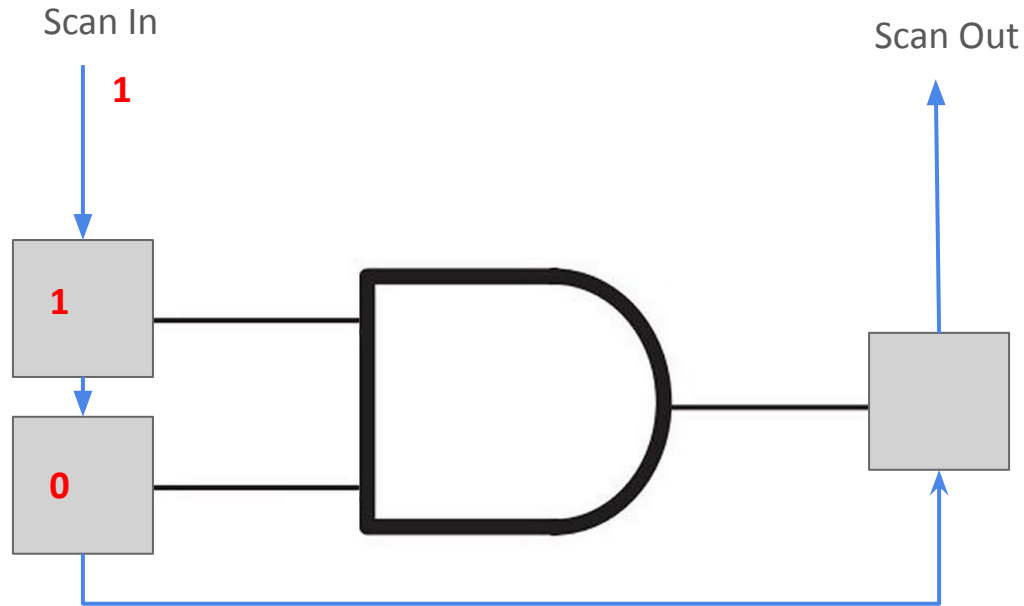Example: Test And Gate



- Enable Scan
- **Shift in 011 (MSB)**
- Disable Scan
- Step the clock
- Enable Scan
- Check for **1** on scan out



Scan Chain Example

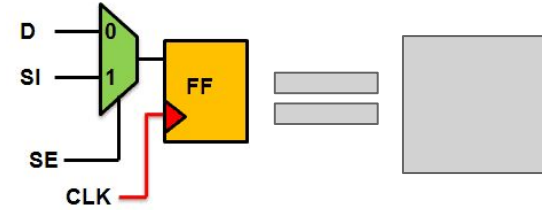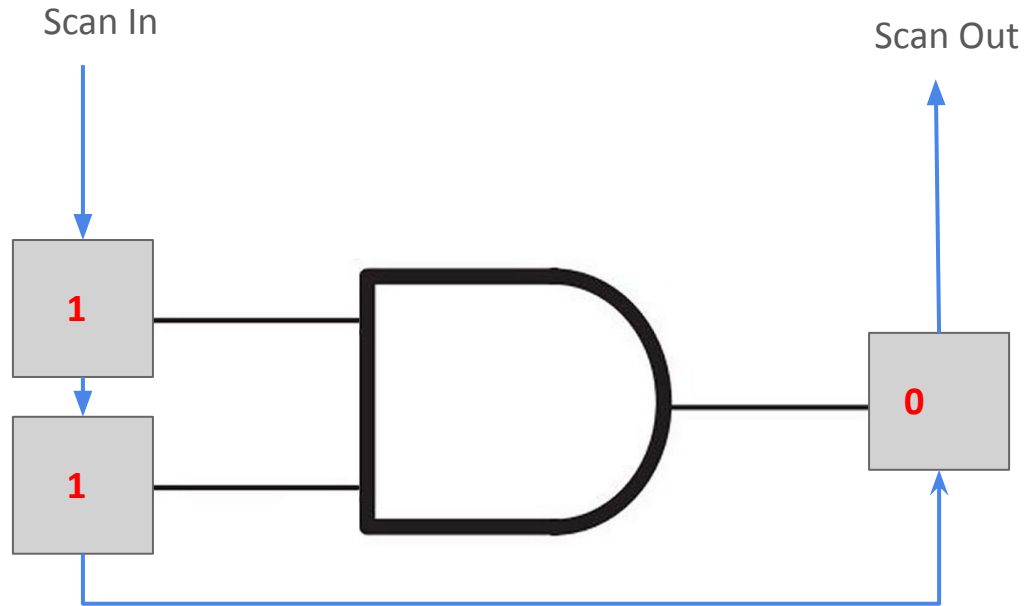Example: Test And Gate



- Enable Scan
- **Shift in 011 (MSB)**
- Disable Scan
- Step the clock
- Enable Scan
- Check for **1** on scan out



Scan Chain Example

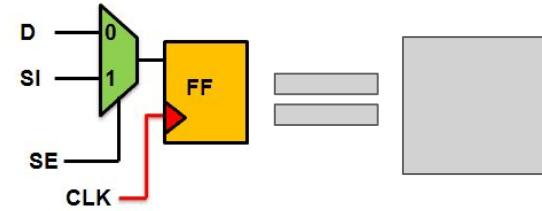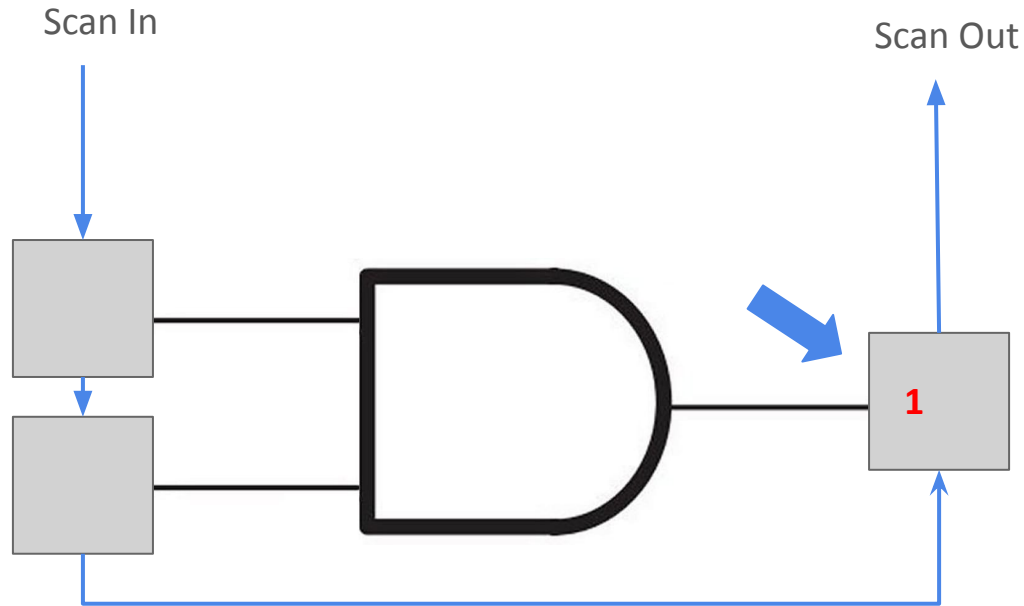Example: Test And Gate



- Enable Scan
- Shift in 011 (MSB)
- Disable Scan
- **Step the clock**
- Enable Scan
- Check for 1 on scan out




Scan Chain Example

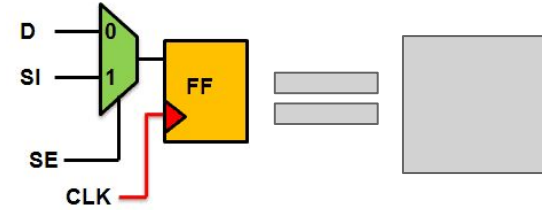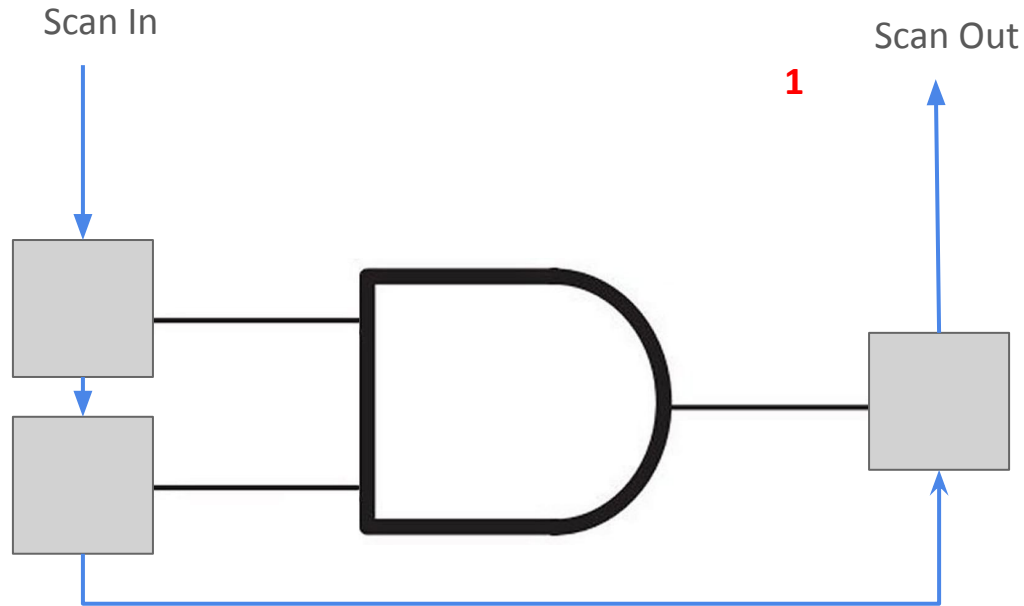Example: Test And Gate

- Enable Scan
- Shift in 011 (MSB)
- Disable Scan
- Step the clock
- Enable Scan
- **Check for 1 on scan out**



Scan Chain Overhead

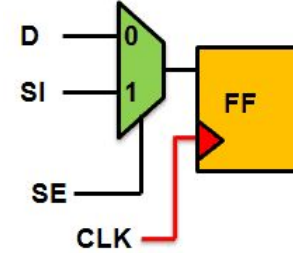

- Overhead: Add 1 mux and 2 wires (SI, SE) to every single flip flop
 - This is not cheap!
 - Shift registers are prone to hold violations → Need extra buffers to fix
- Usually adds between 1 and 10% maximum area
- Makes routing more congested

Circuit	Original RTL (before scan insertion)	Total Area		Area Overhead	
		<i>RTL</i> <i>scan</i>	<i>GL scan</i>	<i>RTL</i> <i>scan</i>	<i>GL</i> <i>scan</i>
FIR	3219.67	3341.72	3506.59	5.12 %	8.91 %
IIR	8038.32	8321.10	8442.74	3.52 %	5.03 %

ATPG

- **ATPG** algorithmically generates test patterns to find faults
 - Hundreds Millions of flip flops
 - 2 states each
 - cannot just test every possible state
 - Must make smart decisions about what to test
 - SAT solvers used to find optimal tests


Bring-Up Testing:

- Use **ATE** to inject patterns at high speed
 - Physical hardware connected to physical chip

Glossary



ATPG: Automatic Test Pattern Generation

ATE: Automatic Test Equipment

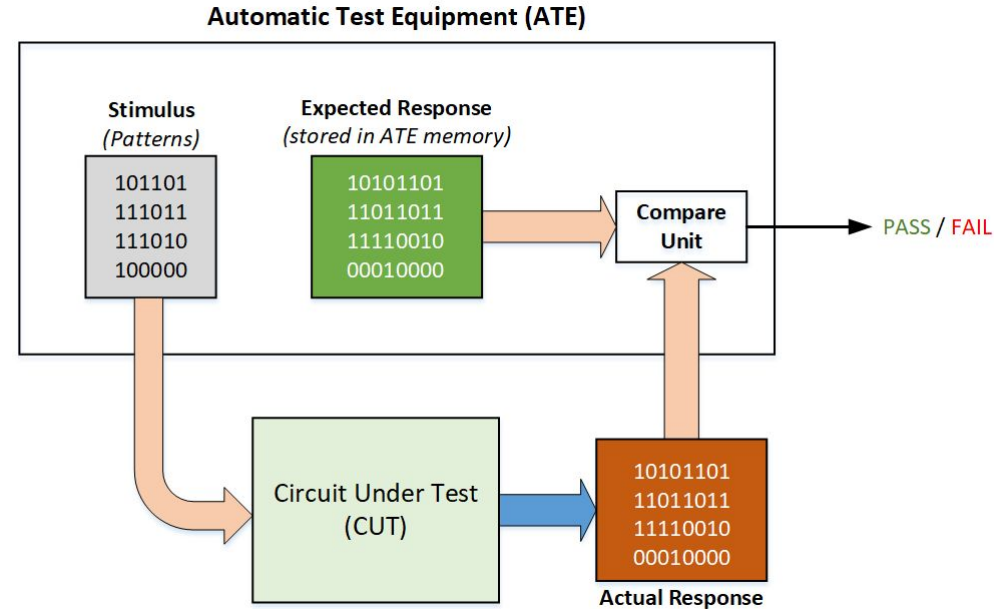

Fault Types

- **Stuck-At** Faults: gate is shorted high or low
 - Gate always outputs 1 or 0
 - Will appear correct sometimes
 - Need to test cases such that both outputs are tested
 - Ex: Stuck-At-1 Nand Gate appears correct $\frac{3}{4}$ of the time
- **At-Speed** Faults: only show up in certain situations, frequency dependent
 - Slow-To-Rise: only shows up on transition from 0 to 1
 - Slow-To-Fall: only on 1 to 0
- At-Speed faults require tests spanning multiple clock cycles, to force a transition

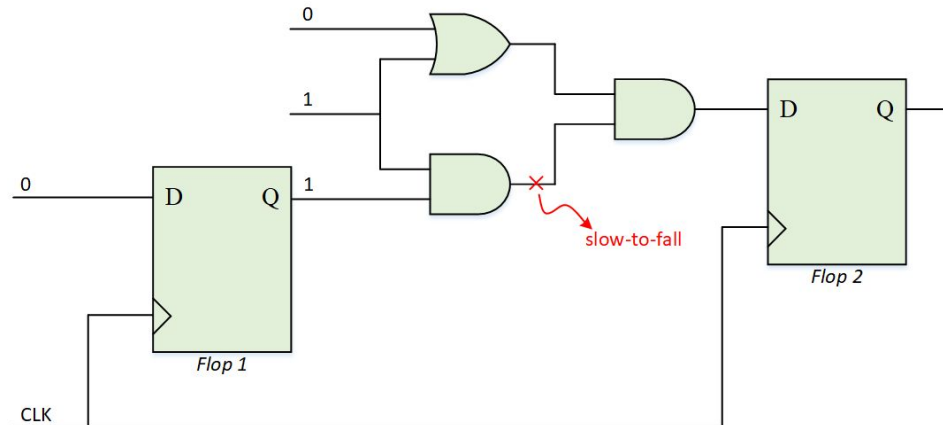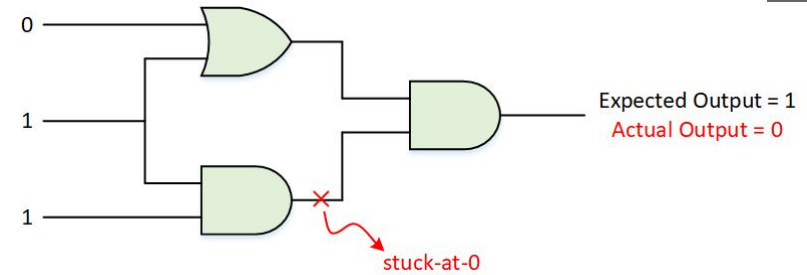


JTAG

Glossary


JTAG: Joint Test Action Group

TAP: Test Access Port

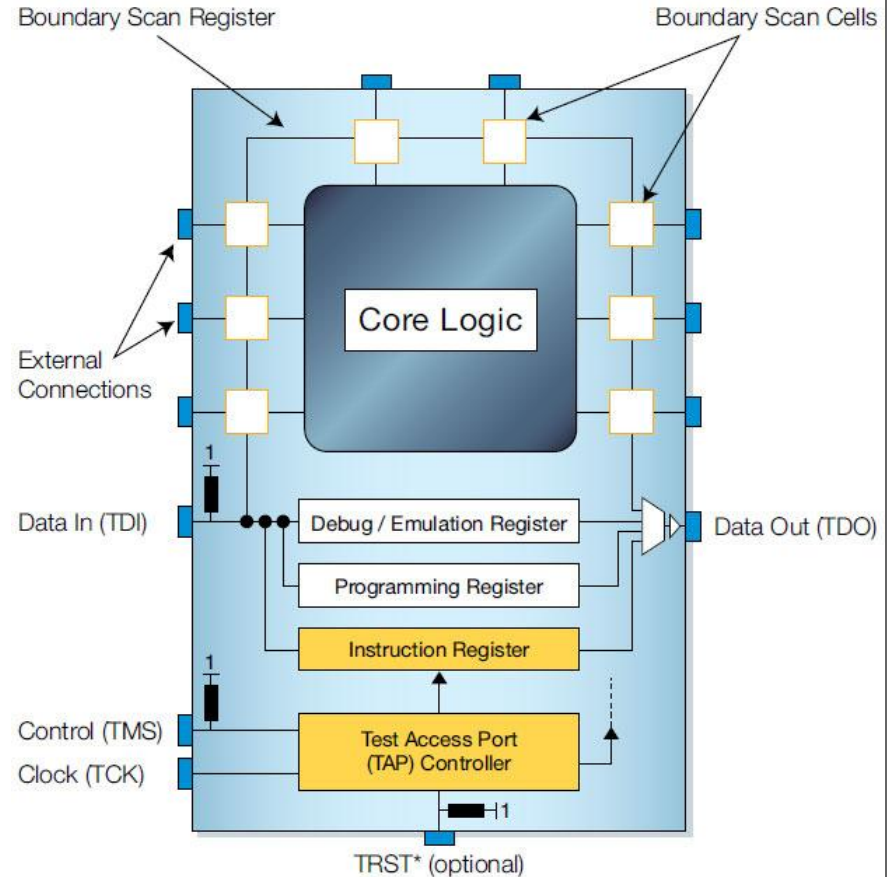- **JTAG** introduces industry standard way of verifying ICs and PCBs after manufacture
 - Find issues with PCB to IC connections
 - Defines standardized interface
- **Boundary Scan:** scan chain only connected to each IO Pins, exposed over JTAG
 - Enables reading each IO pin automatically
- **TAP** has a small FSM that:
 - takes instructions
 - exposes the boundary scan
 - runs tests



Fault DFT

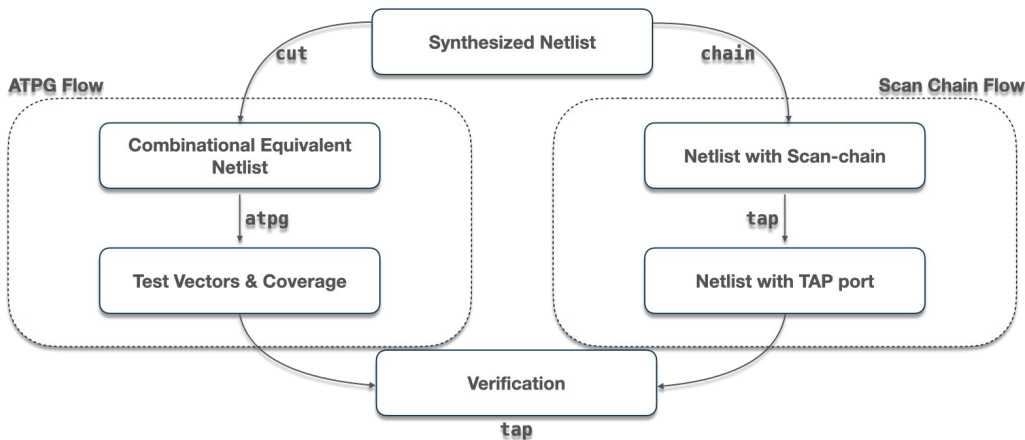

- Open Source DFT toolchain
 - Scanchain and ATPG
- Written in Swift
 - Same language as IOS apps
- Developed by American University in Cairo's Open Source Hardware Lab
 - Same group behind DFFRAM
- Cuts each flip flop out of netlist, adds mux and scan enable
- Integration with Openlane still in progress

References

- <https://anysilicon.com/overview-and-dynamics-of-scan-testing/>
- https://www.researchgate.net/publication/375688367_ASIC_Implementation_for_Multiple_Scan_at_Register_Transfer_Level
- <https://ieeexplore.ieee.org/document/9324799>
- <https://www.xjtag.com/about-jtag/what-is-jtag/>
- <https://vlsitutorials.com/dft-scan-and-atpg/>